

# EECS150 - Digital Design

## Lecture 22 – Carry Look Ahead Adders+ Multipliers

Nov. 12, 2013

Prof. Ronald Fearing

Electrical Engineering and Computer  
Sciences

University of California, Berkeley

(slides courtesy of Prof. John Wawrzynek)

<http://www-inst.eecs.berkeley.edu/~cs150>

Fall 2013

EECS150 - Lec22-CLAdder-mult

Page 1

### Recap

- clocks and timing in Xilinx


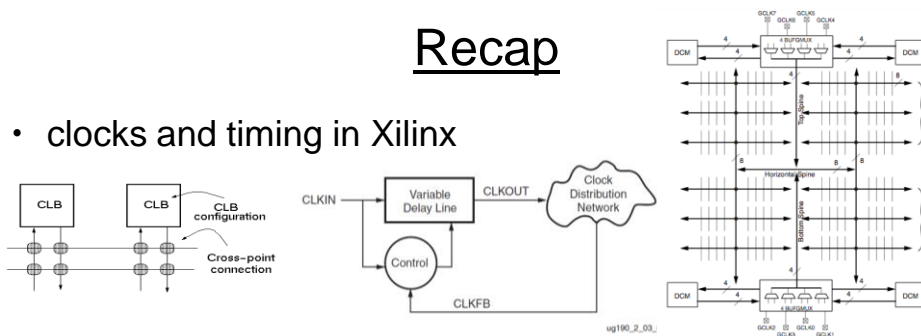


Figure 2-3: Simplified DLL Circuit

- Carry Select Adder

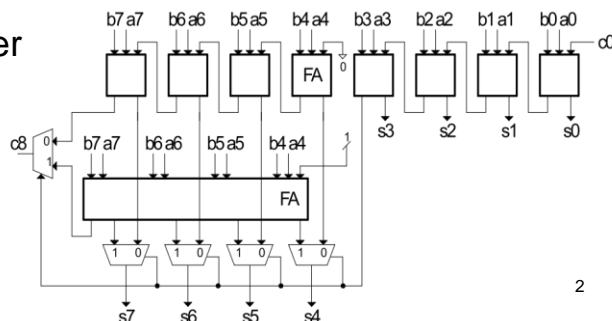


## Outline

- Carry Look-ahead Adder- Can we speed up addition by being clever with carry?
- How can we multiply quickly?

3
 
## Carry Select Adder

- Extending Carry-select to multiple blocks




- What is the optimal # of blocks and # of bits/block?
  - If blocks too small delay dominated by total mux delay
  - If blocks too large delay dominated by adder delay

$\sqrt{N}$  stages of  $\sqrt{N}$  bits

$T \sim \sqrt{N}$ ,  
Cost  $\cong 2 \cdot \text{ripple} + \text{muxes}$

## Carry Select Adder

 

- Compare to ripple adder delay:  
 $T_{\text{total}} = 2 \sqrt{N} T_{\text{FA}} - T_{\text{FA}}$ , assuming  $T_{\text{FA}} = T_{\text{MUX}}$   
 For ripple adder  $T_{\text{total}} = N T_{\text{FA}}$   
 “cross-over” at  $N=3$ , Carry select faster for any value of  $N>3$ .
- Is  $\sqrt{N}$  really the optimum?
  - From right to left increase size of each block to better match match delays
  - Ex: 64-bit adder, use block sizes [12 11 10 9 8 7 7]

Fall 2013


EECS150 - Lec22-CLAdder-mult

Page 5

## Carry Look-ahead Adders

- In general, for n-bit addition best we can achieve is  
 delay  $\sim \log(n)$
- How do we arrange this? (think trees)
- First, reformulate basic adder stage:

a	b	$c_i$	$c_{i+1}$	$s_i$	
0	0	0	0	0	carry “kill” $k_i = a_i' b_i'$
0	0	1	0	1	
0	1	0	0	1	carry “propagate” $p_i = a_i \text{ XOR } b_i$
0	1	1	1	0	
1	0	0	0	1	carry “generate” $g_i = a_i b_i$
1	0	1	1	0	
1	1	0	1	0	
1	1	1	1	1	

 

$$\begin{aligned} c_{i+1} &= g_i + p_i c_i \\ s_i &= p_i \text{ XOR } c_i \end{aligned}$$

Fall 2013


EECS150 - Lec22-CLAdder-mult

Page 6
 
## Carry Look-ahead Adders

- Ripple adder using p and g signals:

$$\begin{aligned} p_i &= a_i \text{ XOR } b_i \\ g_i &= a_i b_i \end{aligned}$$



- So far, no advantage over ripple adder:  $T \sim N$

Fall 2013

EECS150 - Lec22-CLAdder-mult

Page 7

## Carry Look-ahead Adders

- Expand carries:

$$c_0$$

$$c_1 = g_0 + p_0 c_0$$

$$c_2 = g_1 + p_1 c_1 = g_1 + p_1 g_0 + p_1 p_0 c_0$$

$$c_3 = g_2 + p_2 c_2 = g_2 + p_2 g_1 + p_1 p_2 g_0 + p_2 p_1 p_0 c_0$$

$$c_4 = g_3 + p_3 c_3 = g_3 + p_3 g_2 + p_3 p_2 g_1 + \dots$$

.

.

.

$$\begin{aligned} p_i &= a_i \text{ XOR } b_i \\ g_i &= a_i b_i \end{aligned}$$

$$\begin{aligned} c_{i+1} &= g_i + p_i c_i \\ s_i &= p_i \text{ XOR } c_i \end{aligned}$$

- Why not implement these equations directly to avoid ripple delay?
  - Lots of gates. Redundancies (full tree for each).
  - Gate with high # of inputs.
- Let's reorganize the equations.


Fall 2013

EECS150 - Lec22-CLAdder-mult

Page 8
 
## Carry Look-ahead Adders

- “Group” propagate and generate signals:



- P true if the group as a whole propagates a carry to  $c_{out}$
- G true if the group as a whole generates a carry


$$C_{out} = G + PC_{in}$$

- Group P and G can be generated hierarchically.

Fall 2013

EECS150 - Lec22-CLAdder-mult


Page 9

 

Fall 2013


EECS150 - Lec22-CLAdder-mult

Page 10

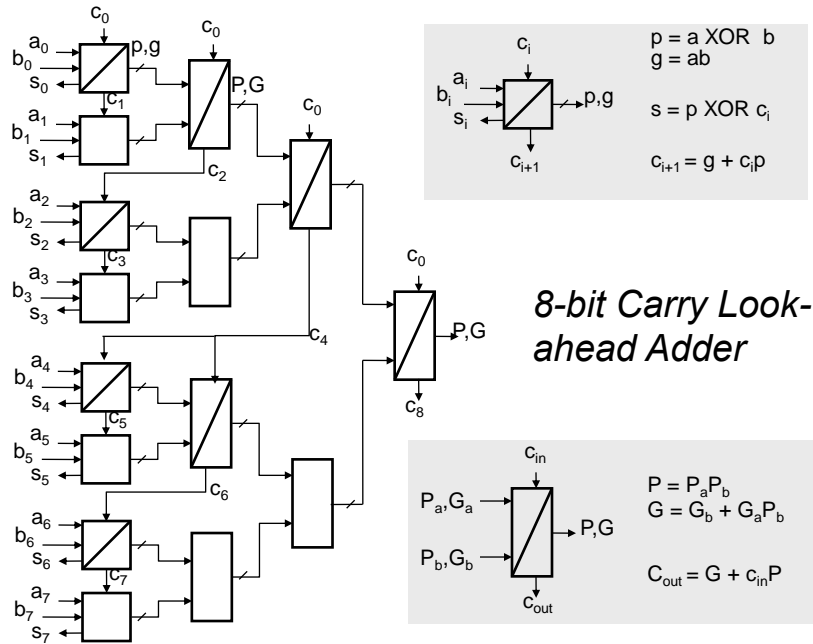 

Fall 2013

EECS150 - Lec22-CLAdder-mult

Page<sub>11</sub>

Fall 2013


EECS150 - Lec22-CLAdder-mult

Page<sub>12</sub>



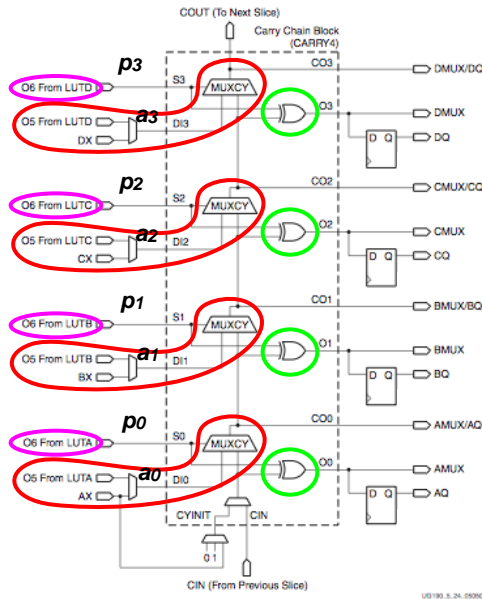
# Virtex 5 Vertical Logic

$$\begin{aligned} p_i &= a_i \text{ XOR } b_i \\ g_i &= a_i b_i \end{aligned}$$



 We can map ripple-carry addition onto carry-chain block.



a	b	$c_i$	$c_{i+1}$	s
0	0	0	0	0
0	0	1	0	1
0	1	0	1	1
0	1	1	1	0
1	0	0	1	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1


$$c_{out} = p_i c_{in} \text{ OR } a_i b_i$$

$$p_i = a_i \text{ XOR } b_i$$

The carry-chain block also useful for speeding up other adder structures and counters.

$$\begin{aligned} c_{i+1} &= g_i + p_i c_i \\ s_i &= p_i \text{ XOR } c_i \end{aligned}$$

## Bit-serial Adder

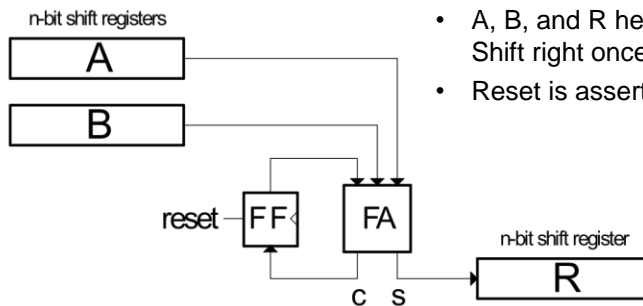

- A, B, and R held in shift-registers. Shift right once per clock cycle.
- Reset is asserted by controller.

- Addition of 2 n-bit numbers:
  - takes n clock cycles,
  - uses 1 FF, 1 FA cell, plus registers
  - the bit streams may come from or go to other circuits, therefore the registers might not be needed.



## Adder Final Words

Type	Cost	Delay
Ripple	$O(N)$	$O(N)$
Carry-select	$O(N)$	$O(\sqrt{N})$
Carry-lookahead	$O(N)$	$O(\log(N))$

- Dynamic energy per addition for all of these is  $O(n)$ .
- “O” notation hides the constants. Watch out for this!
- The “real” cost of the carry-select is at least 2X the “real” cost of the ripple. “Real” cost of the CLA is probably at least 2X the “real” cost of the carry-select.
- The actual multiplicative constants depend on the implementation details and technology.
- FPGA and ASIC synthesis tools will try to choose the best adder architecture automatically - assuming you specify addition using the “+” operator, as in “`assign A = B + C`”

Fall 2013

EECS150 – Lec21-timing-adder

Page<sub>17</sub>

## Multiplication

$$\begin{array}{rcccccl}
 & & a_3 & a_2 & a_1 & a_0 & \leftarrow \text{Multiplicand} \\
 & & b_3 & b_2 & b_1 & b_0 & \leftarrow \text{Multiplier} \\
 & & \hline
 & X & a_3b_0 & a_2b_0 & a_1b_0 & a_0b_0 & \\
 & & a_3b_1 & a_2b_1 & a_1b_1 & a_0b_1 & \\
 & & a_3b_2 & a_2b_2 & a_1b_2 & a_0b_2 & \\
 a_3b_3 & a_2b_3 & a_1b_3 & a_0b_3 & & & \\
 & & \hline
 & & \dots & a_1b_0 + a_0b_1 & a_0b_0 & & \leftarrow \text{Product}
 \end{array}$$

} *Partial products*


*Many different circuits exist for multiplication.  
 Each one has a different balance between **speed**  
 (**performance**) and amount of **logic** (cost).*

Fall 2013

EECS150 - Lec22-CLAdder-mult

Page<sub>18</sub>

## “Shift and Add” Multiplier

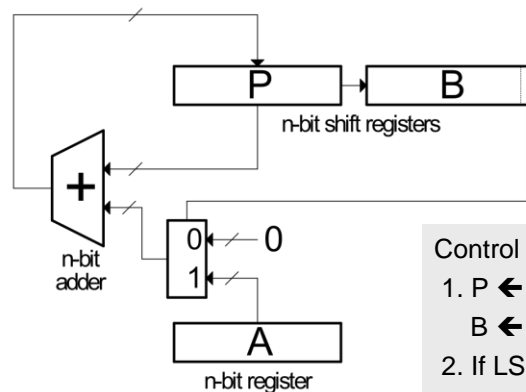

- Sums each partial product, one at a time.
- In binary, each partial product is shifted versions of A or 0.

### Control Algorithm:

1.  $P \leftarrow 0$ ,  $A \leftarrow$  multiplicand,  $B \leftarrow$  multiplier
2. If LSB of  $B == 1$  then add  $A$  to  $P$   
else add 0
3. Shift  $[P][B]$  right 1
4. Repeat steps 2 and 3  $n-1$  times.
5.  $[P][B]$  has product.

- Cost  $\sim n$ ,  $T = n$  clock cycles.
- What is the critical path for determining the min clock period?

Fall 2013

EECS150 - Lec22-CLAdder-mult

Page19

## “Shift and Add” Multiplier

### Signed Multiplication:

*Remember* for 2's complement numbers MSB has negative weight:

$$X = \sum_{i=0}^{N-2} x_i 2^i - x_{n-1} 2^{n-1}$$

$$\begin{aligned} \text{ex: } -6 &= 11010_2 = 0 \cdot 2^0 + 1 \cdot 2^1 + 0 \cdot 2^2 + 1 \cdot 2^3 - 1 \cdot 2^4 \\ &= 0 + 2 + 0 + 8 - 16 = -6 \end{aligned}$$

- Therefore for multiplication:
  - a) subtract final partial product
  - b) sign-extend partial products
- Modifications to shift & add circuit:
  - a) adder/subtractor
  - b) sign-extender on P shifter register


Fall 2013

EECS150 - Lec22-CLAdder-mult

Page20
 
## Bit-serial Multiplier

- Bit-serial multiplier ( $n^2$  cycles, one bit of result per  $n$  cycles):



- Control Algorithm:

```

repeat n cycles { // outer (i) loop
  repeat n cycles{ // inner (j) loop
    shiftA, selectSum, shiftHI
  }
  shiftB, shiftHI, shiftLOW, reset
}

```

**Note:** The occurrence of a control signal  $x$  means  $x=1$ . The absence of  $x$  means  $x=0$ .


Fall 2013

EECS150 - Lec22-CLAdder-mult

Page21

## Array Multiplier

Single cycle multiply: Generates all  $n$  partial products simultaneously.

 

Fall 2013

EECS150 - Lec22-CLAdder-mult

Page22

## Carry-Save Addition


- Speeding up multiplication is a matter of speeding up the summing of the partial products.
  - “Carry-save” addition can help.
  - Carry-save addition passes (saves) the carries to the output, rather than propagating them.
- Example: sum three numbers,  $3_{10} = 0011$ ,  $2_{10} = 0010$ ,  $3_{10} = 0011$
- |                       |          |      |          |          |
|-----------------------|----------|------|----------|----------|
|                       |          | 0000 | carry in |          |
| $3_{10}$              |          | 0011 |          |          |
| +                     | $2_{10}$ | 0010 |          |          |
|                       | c        | 0100 | =        | $4_{10}$ |
|                       | s        | 0001 | =        | $1_{10}$ |
| } carry-save add      |          |      |          |          |
|                       | $3_{10}$ | 0011 |          |          |
|                       | c        | 0010 | =        | $2_{10}$ |
|                       | s        | 0110 | =        | $6_{10}$ |
|                       |          | 1000 | =        | $8_{10}$ |
| } carry-propagate add |          |      |          |          |
- In general, *carry-save* addition takes in 3 numbers and produces 2.
  - Whereas, *carry-propagate* takes 2 and produces 1.
  - With this technique, we can avoid carry propagation until final addition

Fall 2013

EECS150 - Lec22-CLAdder-mult

Page23

## Carry-save Circuits

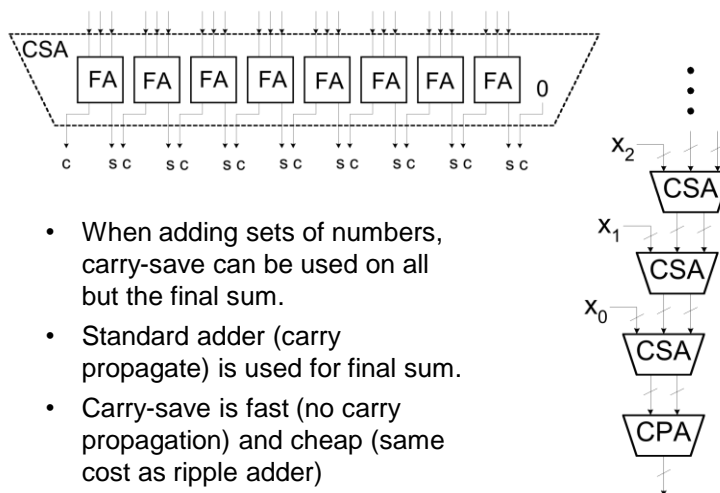


- When adding sets of numbers, carry-save can be used on all but the final sum.
- Standard adder (carry propagate) is used for final sum.
- Carry-save is fast (no carry propagation) and cheap (same cost as ripple adder)

Fall 2013

EECS150 - Lec22-CLAdder-mult

Page24

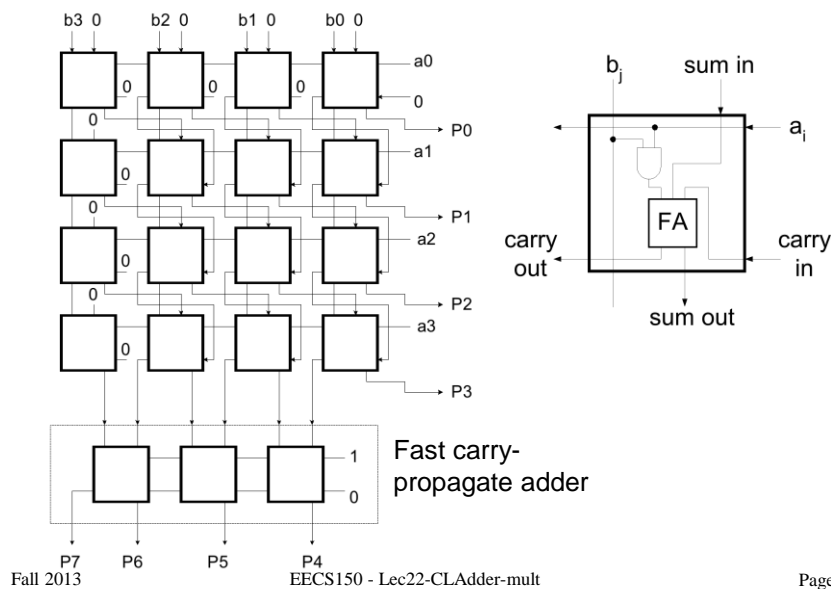
## Array Multiplier using Carry-save Addition


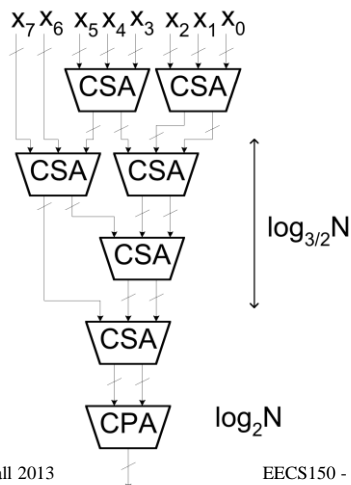
## Carry-save Addition

CSA is associative and commutative. For example:

$$(((X_0 + X_1) + X_2) + X_3) = ((X_0 + X_1) + (X_2 + X_3))$$



- A balanced tree can be used to reduce the logic delay.
- This structure is the basis of the **Wallace Tree Multiplier**.
- Partial products are summed with the CSA tree. Fast CPA (ex: CLA) is used for final sum.
- Multiplier delay  $< \log_{3/2} N + \log_2 N$

## Constant Multiplication

- Our discussion so far has assumed both the multiplicand (A) and the multiplier (B) can vary at runtime.
- What if one of the two is a constant?

$$Y = C * X$$

- “Constant Coefficient” multiplication comes up often in signal processing and other hardware. Ex:

$$y_i = \alpha y_{i-1} + x_i \quad x_i \rightarrow \boxed{\phantom{00}} \rightarrow y_i$$

where  $\alpha$  is an application dependent constant that is hard-wired into the circuit.

- How do we build an array style (combinational) multiplier that takes advantage of the constancy of one of the operands?


Fall 2013

EECS150 - Lec22-CLAdder-mult

Page27
 
## Multiplication by a Constant

- If the constant C in  $C * X$  is a power of 2, then the multiplication is simply a shift of X.
- Ex:  $4 * X$



- What about division?
- What about multiplication by non-powers of 2?


Fall 2013

EECS150 - Lec22-CLAdder-mult


Page28
 
## Multiplication by a Constant

- In general, a combination of fixed shifts and addition:
  - Ex:  $6 * X = 0110 * X = (2^2 + 2^1) * X$



– Details:

 


Fall 2013

EECS150 - Lec22-CLAdder-mult

Page29
 
## Multiplication by a Constant

- Another example:  $C = 23_{10} = 010111$



- In general, the number of additions equals the number of 1's in the constant minus one.*
- Using carry-save adders (for all but one of these) helps reduce the delay and cost, but the number of adders is still the number of 1's in  $C$  minus 2.
- Is there a way to further reduce the number of adders (and thus the cost and delay)?


Fall 2013

EECS150 - Lec22-CLAdder-mult

Page30

## Multiplication using Subtraction

- *Subtraction is ~ the same cost and delay as addition.*
- Consider  $C \cdot X$  where  $C$  is the constant value  $15_{10} = 01111_2$ .  
 $C \cdot X$  requires 3 additions.
- We can “recode” 15  
 from  $01111 = (2^3 + 2^2 + 2^1 + 2^0)$   
 to  $1000\bar{1} = (2^4 - 2^0)$   
 where  $\bar{1}$  means negative weight.
- Therefore,  $15 \cdot X$  can be implemented with only one subtractor.

 

Fall 2013

EECS150 - Lec22-CLAdder-mult

Page31

## Canonic Signed Digit Representation

- CSD represents numbers using 1,  $\bar{1}$ , & 0 with the least possible number of non-zero digits.
  - Strings of 2 or more non-zero digits are replaced.
  - Leads to a unique representation.
- To form CSD representation might take 2 passes:
  - First pass: replace all occurrences of 2 or more 1's:  
 $01..10$  by  $10..\bar{1}0$
  - Second pass: same as above, plus replace  $0110$  by  $0010$
- Examples:

$$011101 = 29$$

$$100\bar{1}01 = 32 - 4 + 1$$

$$0010111 = 23$$

$$001100\bar{1}$$

$$010\bar{1}00\bar{1} = 32 - 8 - 1$$

$$0110110 = 54$$

$$10\bar{1}10\bar{1}0$$

$$100\bar{1}0\bar{1}0 = 64 - 8 - 2$$

- Can we further simplify the multiplier circuits?

Fall 2013


EECS150 - Lec22-CLAdder-mult

Page32



 
## “Constant Coefficient Multiplication” (KCM)


Binary multiplier:  $Y = 231 * X = (2^7 + 2^6 + 2^5 + 2^2 + 2^1 + 2^0) * X$



 - CSD helps, but the multipliers are limited to shifts followed by adds.
  - CSD multiplier:  $Y = 231 * X = (2^8 - 2^5 + 2^3 - 2^0) * X$



 - How about shift/add/shift/add ...?
  - KCM multiplier:  $Y = 231 * X = 7 * 33 * X = (2^3 - 2^0) * (2^5 + 2^0) * X$



- No simple algorithm exists to determine the optimal KCM representation.
- Most use exhaustive search method.

Fall 2013


EECS150 - Lec22-CLAdder-mult

Page33



## Summary

- Carry Look-ahead Adder

Carry save adder

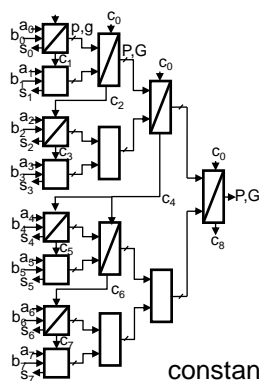

constant coefficient multiplication

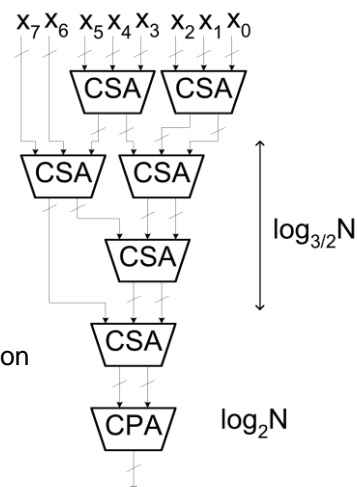 

34